



MILITARY INSTITUTE OF SCIENCE AND TECHNOLOGY

Department of Computer Science and
Engineering

Course Title: Electronic Devices and Circuits
Sessional

Course code: EECE-170


ASSIGNMENT - 2

Mehnaj Hridi

202214068

CSE 22

Lab Evaluation Problems:

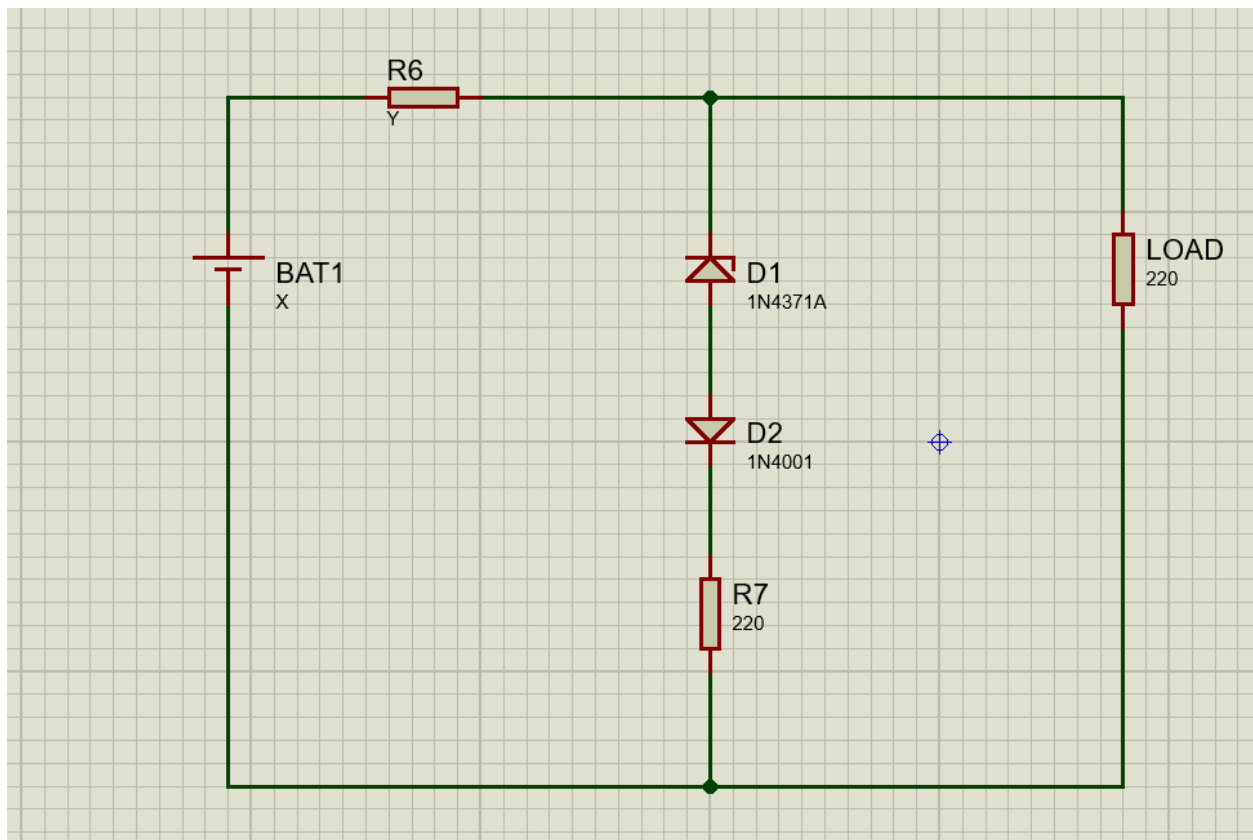



Question no 1:

For what battery voltage will the load current be 22mA, if $Y=220\ \Omega$?

Ans:

Given,

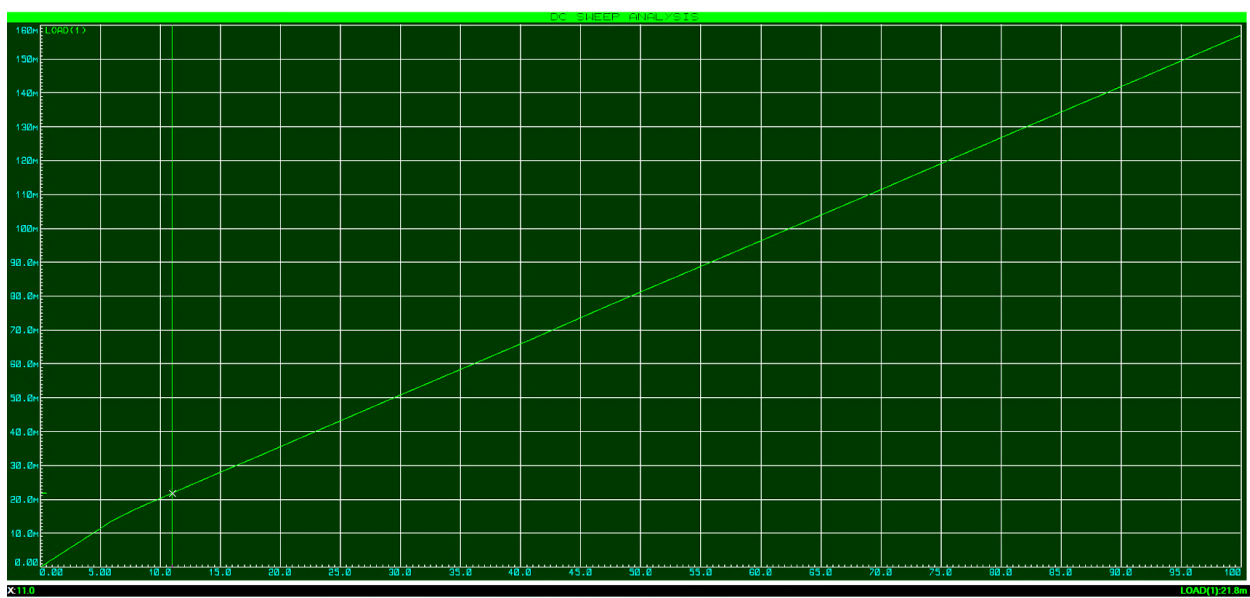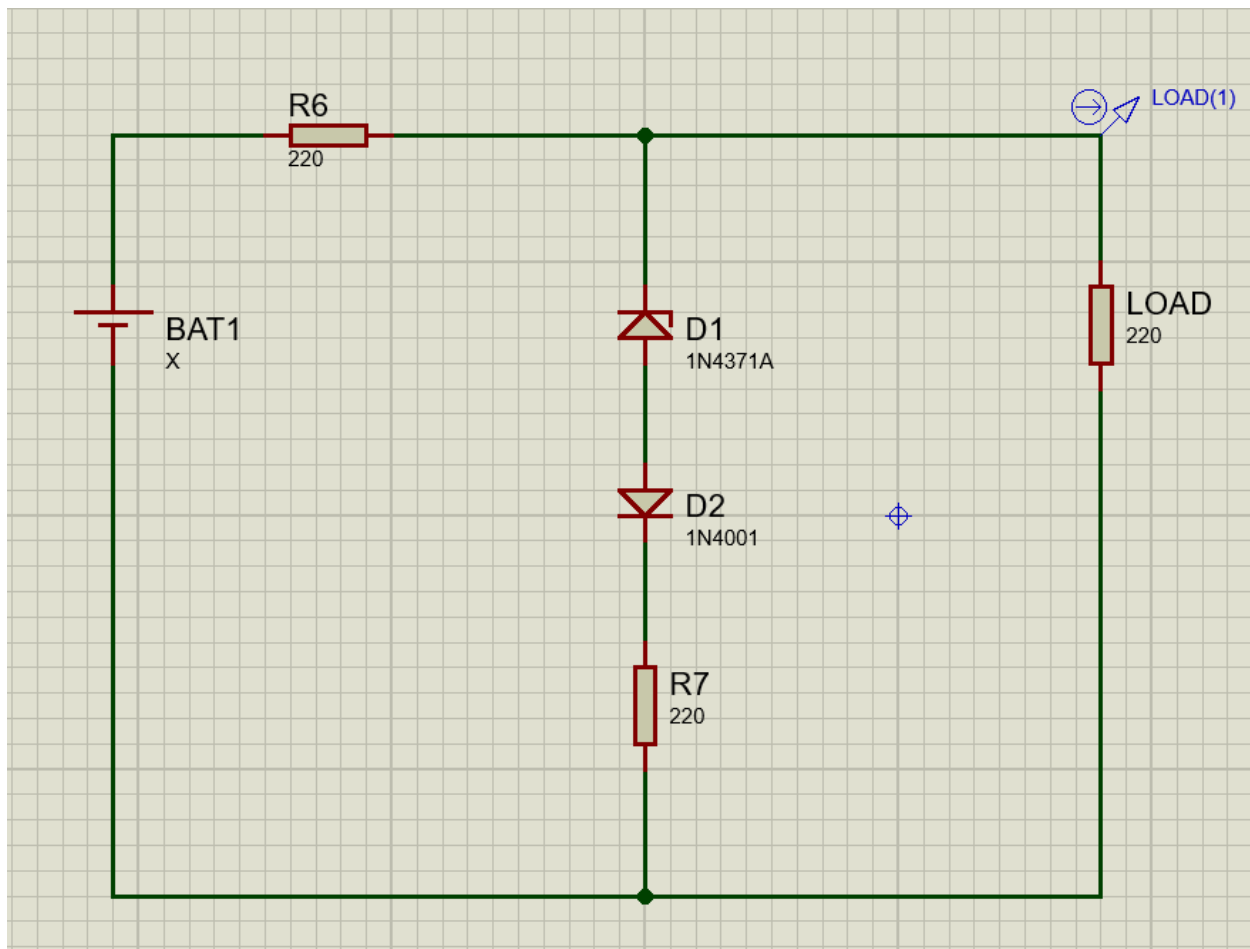$Y=220\ \Omega$, Load current = 22mA, battery voltage=?



From the graph:

Battery voltage = 11V (approximately)

Question No 2:

For what value of Y, when X=9V, will the load power be 40mW?

Ans:

Given, X=9V


Load power, $P = 40\text{mw} = 40 \times 10^{-3}\text{W}$


Load resistance = 220 ohm

We know ,

$$P = i^2 R$$

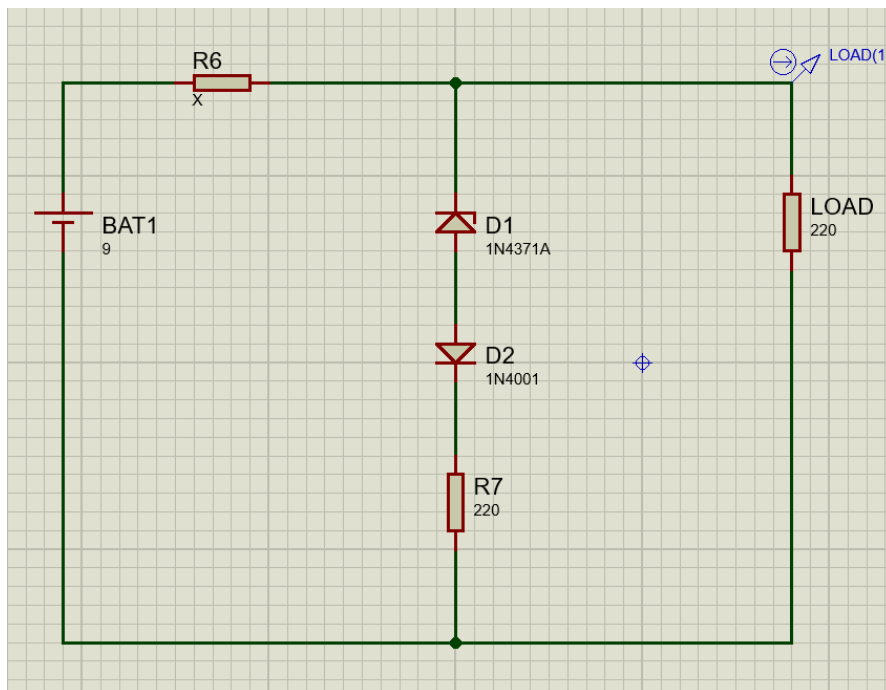Therefore, $i = \text{load current} = 13.48\text{mA}$




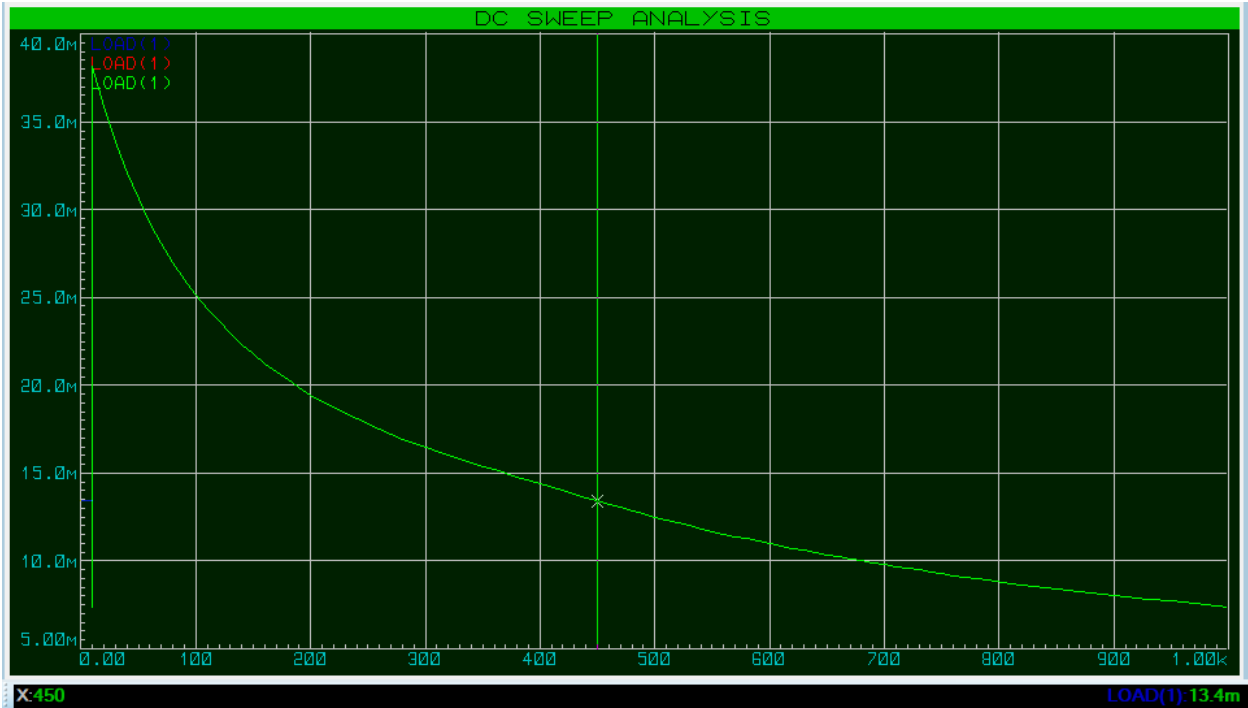


From the graph we get $Y=450\Omega$ when current is 13.4mA.

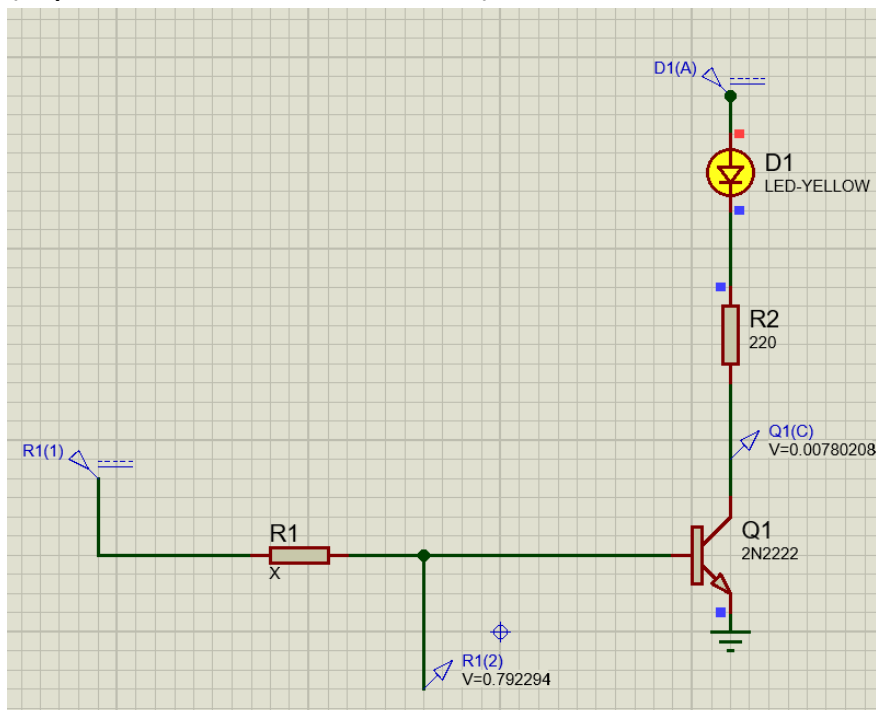
Question 3:

Ans: There are two types of biasing method done in last class in BJT (Bipolar Junction Transistor).



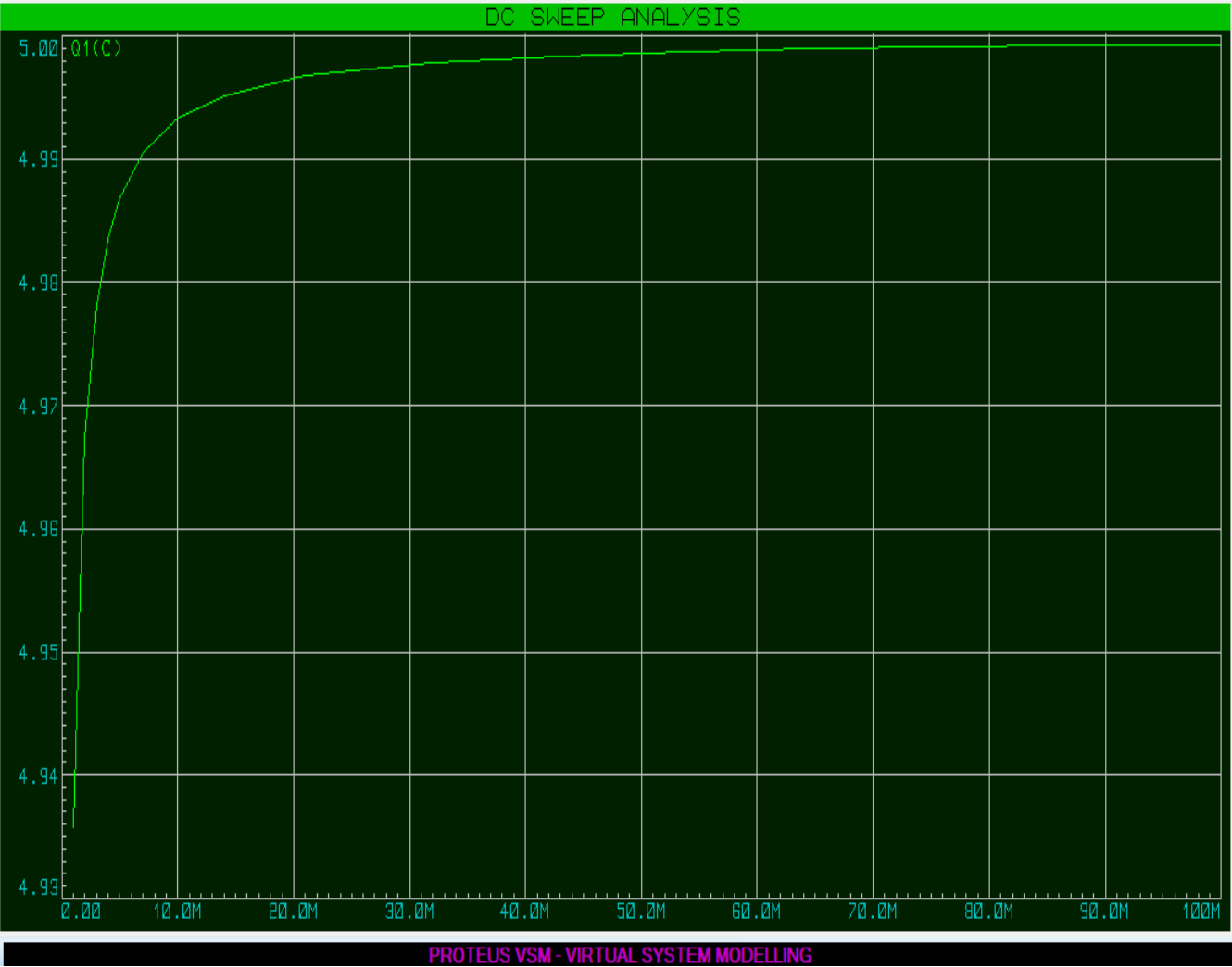

Another method:

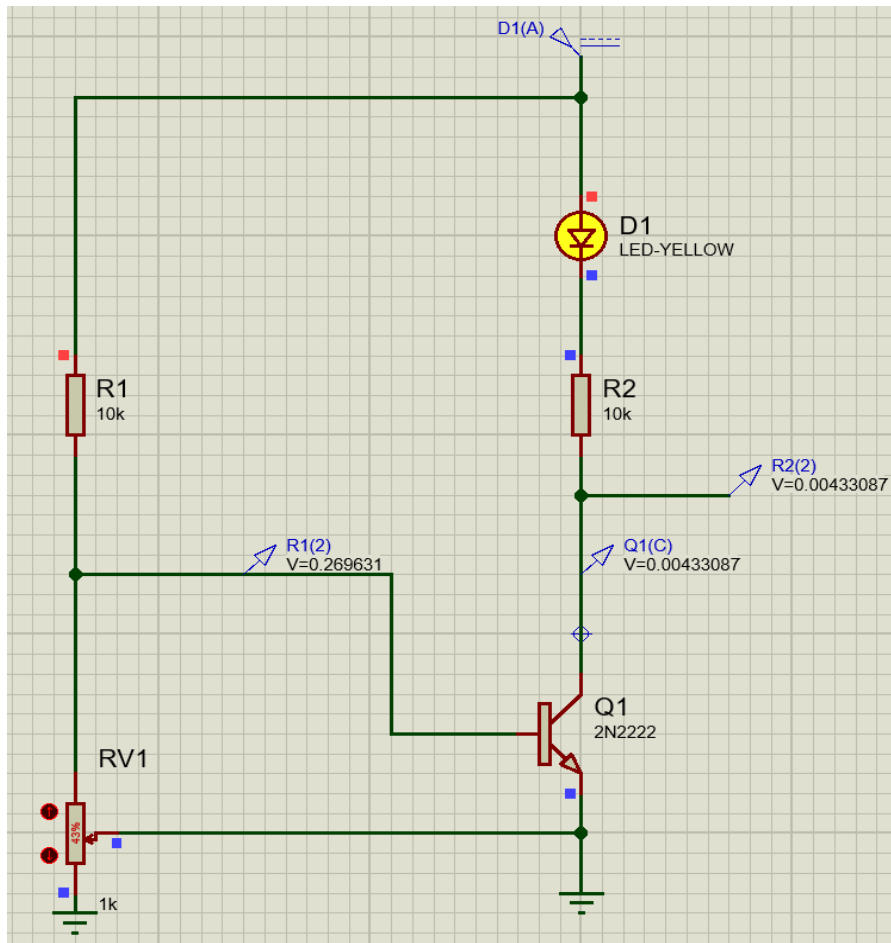

Without Pot-HG:

